


①

Lecture 16

1 OCT 2014

continuing w/ Chapter 25 - Capacitors

Capacitors in a Parallel Configuration

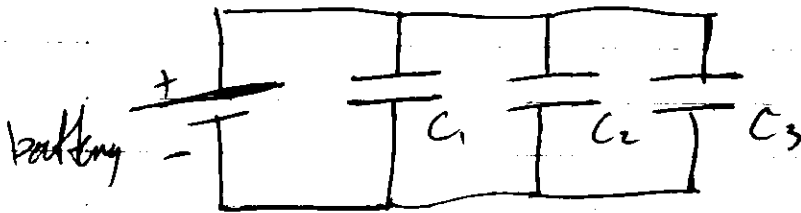

want to replace them w/
an "equivalent capacitor" that
has the same capacitance as
the combination of capacitors.
can be helpful in the design of electrical
circuits.


Important thing to remember about conductors:

charges arrange themselves in such a way
that E-field inside conductor is zero

⇒ all points inside conductor have the
same potential.

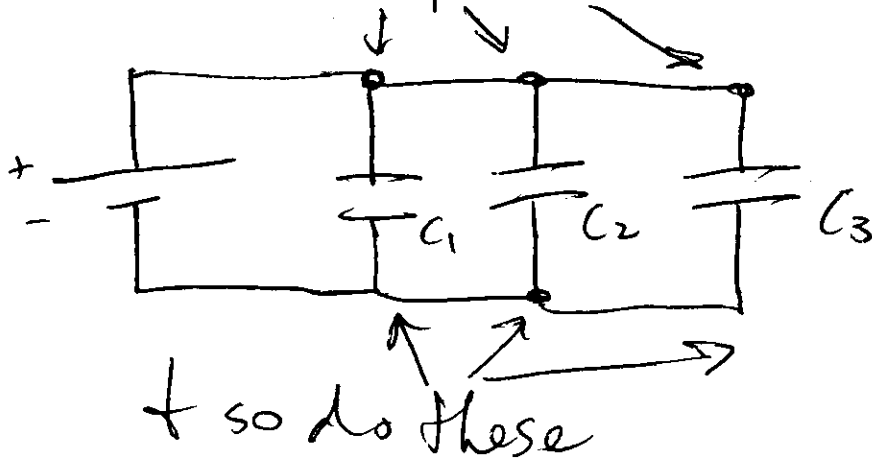(2)

So these ~~points~~ ^{locations} have the same potential



⇒ potential difference across each capacitor is the same

So if it is V across battery, then it is V across each capacitor.

geometries of each capacitor could be different

⇒ ~~capacitors~~

in general, $C_1 \neq C_2 \neq C_3$

but $q_1 = VC_1$, $q_2 = VC_2$ & $q_3 = VC_3$

+ total charge on + side is

$$q = q_1 + q_2 + q_3$$

(3)

So the equivalent capacitor
has charge q +
potential difference V

So its capacitance is given by

$$q = VC$$

$$\Rightarrow q_1 + q_2 + q_3 = VC$$


$$\Rightarrow VC_1 + VC_2 + VC_3 = VC$$

$$\Rightarrow C = C_1 + C_2 + C_3$$

So for capacitors in a parallel
configuration, equivalent capacitor
has capacitance equal to the
sum of the individual ones.

4

Capacitors in a series configuration

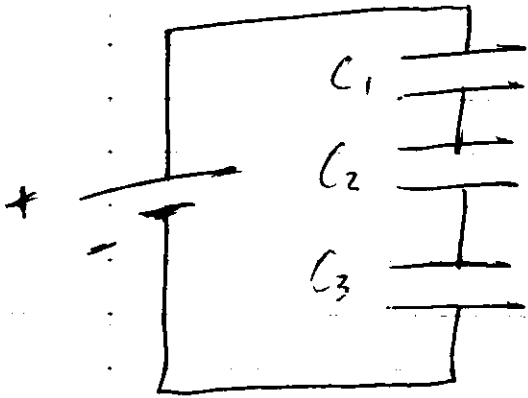

When ~~a~~ battery applies a potential difference, each capacitor ends up w/ the same charge.

Why is this?


a "chain reaction" occurs in which each capacitor charges the next.

1. When battery is connected, electrons from its negative terminal ~~are~~ are repelled & go to bottom plate of C_3 . So this acquires a charge of $-q$.
2. Negative charges on top plate are repelled & go to bottom plate of C_2 , leaving a charge of $+q$ on top plate of C_3 & creating

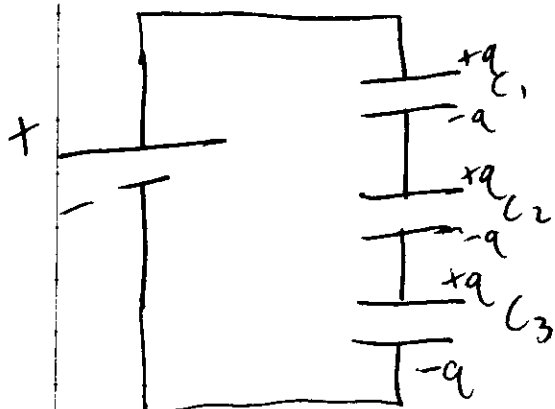(5)

- q charge on bottom plate of C_2 .

- This continues for C_2 to C_1 if
we're left w/



Call potential
difference across
 C_1 as V_1

+ same for
 V_2 + V_3

If potential difference across battery is

$$V, \text{ then } V = V_1 + V_2 + V_3$$

$$\text{using that } V_1 = \frac{q}{C_1}, V_2 = \frac{q}{C_2}, V_3 = \frac{q}{C_3}$$

$$\Rightarrow V = q \left[\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

but change for equivalent capacitor

$$\text{is } q \text{ + using } C = \frac{q}{V}, \text{ we get}$$


6

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

or

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

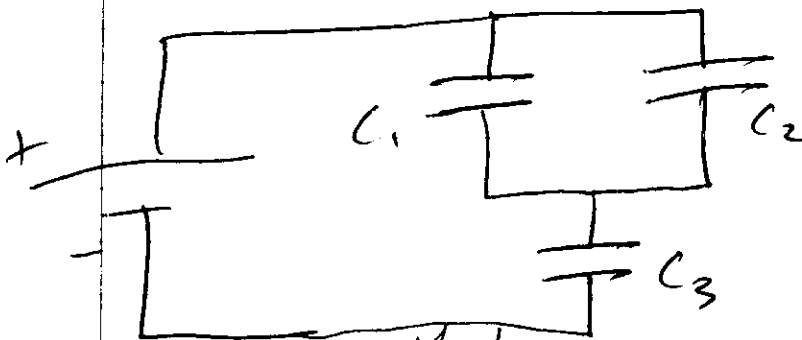QUESTION: How to find potential & charge on each capacitor in the following circuit?



that given battery creates a potential difference of V across its terminals. Idea: find equivalent circuit & mark


7

Energy stored in a capacitor

If we charge up a capacitor, it stores electrical potential energy that can be used to light a light bulb temporarily (for example)

How to quantify the potential energy in a capacitor?

Suppose that we charge a capacitor

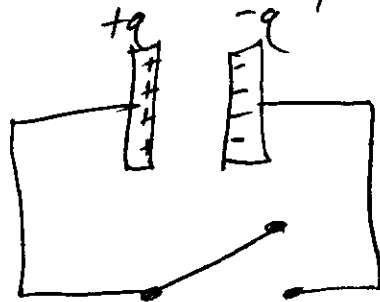

so when it is charged it has potential energy

if we close the circuit, then charge will flow from right plate ~~to~~ around the circuit to left plate

8

Recall that potential is defined in such a way that potential energy is equal to charge q times potential difference V

$$U = qV$$

So one is tempted to say that this is the potential energy of the capacitor ...

The problem w/ this is that as the charge flows from one plate to the other, the potential difference ~~decreases~~ between the plates decreases. So we need to account for this.

We can do so by using calculus

9

Suppose that the charge on capacitor ~~is~~ at some instant is q' . Then the potential difference across the plates at that time instant is

$$V' = \frac{q'}{C}$$

If we then transfer ~~the~~ a differential amount of charge dq' , the little bit of work needed to do so is

$$dW = \frac{q'}{C} dq'$$

To get the total work, we then sum all of these small amounts of work to get

$$\int dW = \int_0^q \frac{q'}{C} dq' = \frac{1}{C} \left[\frac{q'^2}{2} \Big|_0^q \right] = \frac{q^2}{2C}$$

10


So potential energy stored in a capacitor

is
$$U = \frac{q^2}{2C} = \frac{1}{2} CV^2$$

↑ using $q = VC$


Dielectric Material - insert a

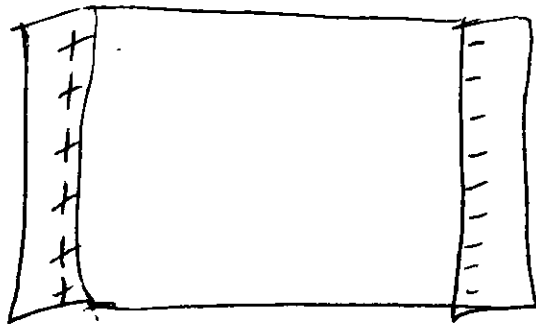nonconducting material between plates of a capacitor to increase the capacitance by a factor $K > 1$



atomic view of what's going on ...

11

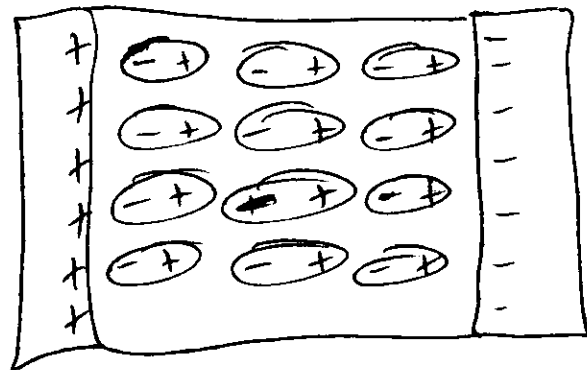

molecules in dielectric material
will polarise all in one direction

there is the E -field ~~set~~ set up
by the plates \longrightarrow

but then the dielectric material
sets up an opposing E -field

\longleftarrow
this has the effect ~~of~~ of
lowering the potential difference
 V of the plates which in turn
raises capacitance b/c

$$C = \frac{q}{V}$$

can quantify this
increase w/ K