

①

Lecture 20

12 OCT 2014

To make charges flow through a resistor, you need a potential difference across its terminals.

To do so, we need a "charge pump" which for historical reasons is called an "EMF device" where EMF is for "electromotive force"

many examples of ~~EMF~~ devices are batteries, electric generators, solar cells, & fuel cells.

(2)


An EMF device does work on positive charge carriers to move them from its - terminal to + terminal

How to calculate the potential difference that an EMF device creates?

Use the "loop rule" for a circuit: The sum of the changes in potential when going around a loop of a circuit is equal to zero. (AKA Kirchhoff voltage law)

similar to walking up a mountain, around, & then returning to the same point (change in potential is zero)

3

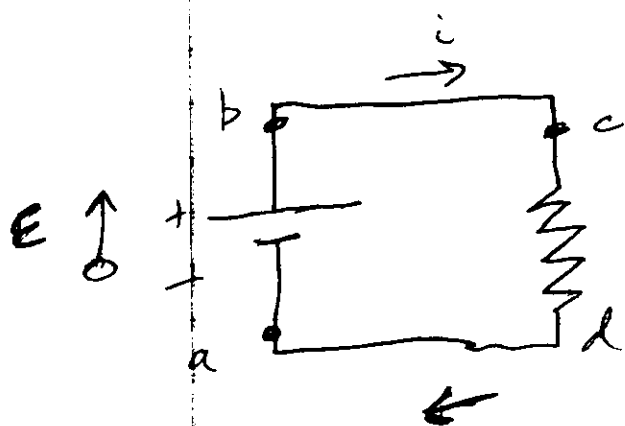

Say that potential @ point a is V_a

going from a to b, potential increase is \mathcal{E} (EMF)

going from c to d, potential @ c is higher than @ d, so change is $-iR$

finally, we end up where ^{we} started, so


$$V_a + \mathcal{E} - iR = V_a$$

$$\Rightarrow \mathcal{E} = iR$$

(4)

Real batteries (EMF devices) have an internal resistance that is unavoidable.

We can model this by

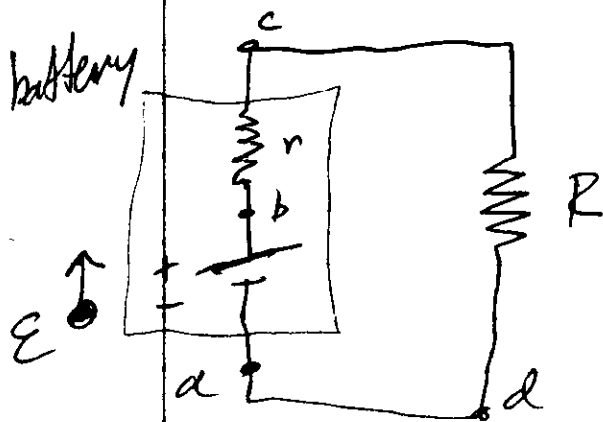

QUESTION:

What is ϵ here?

Just use the same reasoning! ..

(remember that current is constant here due to conservation of charge)

from a to b ~~ε~~ ϵ

b to c $-ir$


c to d $-iR$

$$\Rightarrow \epsilon - ir - iR = 0$$
$$\Rightarrow \epsilon = i(r+R) \Rightarrow i = \frac{\epsilon}{r+R}$$


5

So the internal resistance causes the current to be lower than it should be.

can draw this kind of plot as well

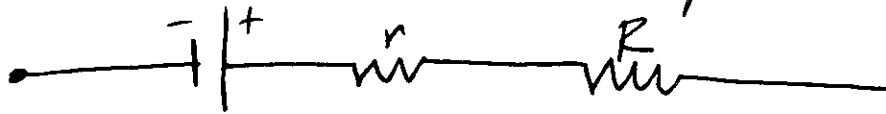


Potential

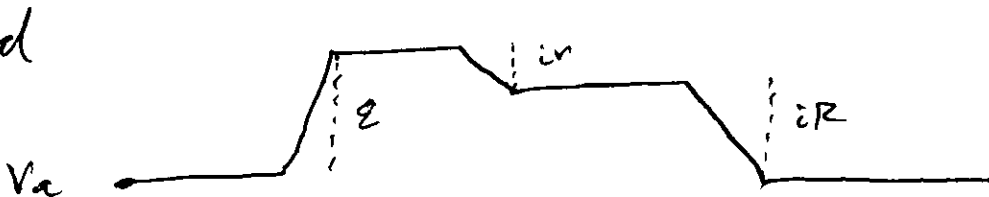

up & down a hill...


Resistors in Series

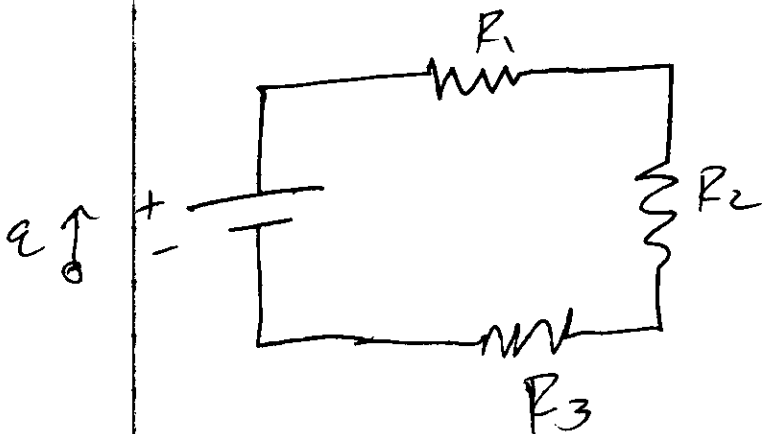

What is the equivalent resistance?

(6)

i.e., find R_{eq} such that

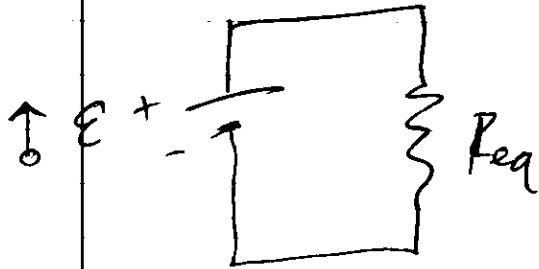

where potential across R_{eq} is the same as that across all three + current through is the same as well

1st, use what we did before

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$

$$\Rightarrow i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$

$$\Rightarrow \frac{\mathcal{E}}{i} = R_1 + R_2 + R_3$$

For equivalent circuit, \mathcal{E} is unchanged + $s = i$

$$\Rightarrow \mathcal{E} - iR_{eq} = 0$$

$$\frac{\mathcal{E}}{i} = R_{eq}$$


$$\Rightarrow R_{eq} = R_1 + R_2 + R_3$$

so for resistors in series, just add them

7

Finding the Potential difference between two points in a circuit

Consider circuit from before:

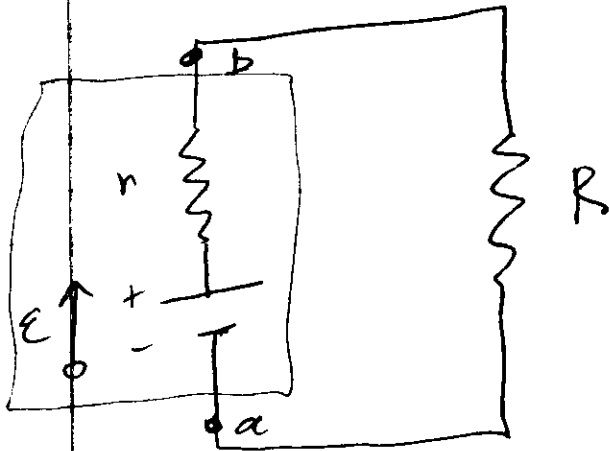

We might want to know the potential difference between a & b

QUESTION: What is $V_a - V_b$?


At ~~a~~ a, say it is V_a & at b, V_b

$$\text{then } V_a + \mathcal{E} - ir = V_b$$

$$\Rightarrow V_b - V_a = \mathcal{E} - ir$$

we found i before to be

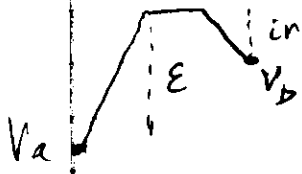
$$i = \frac{\mathcal{E}}{R+r} \Rightarrow \Delta V = \mathcal{E} - \frac{\mathcal{E}}{R+r} r = \frac{\mathcal{E}}{R+r} R$$



8

Power delivered by real batteries

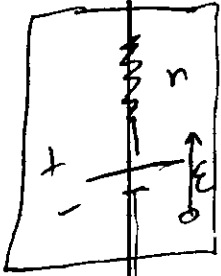$P = iV$ where V is potential difference across terminals



From before,

$$V = \mathcal{E} - ir$$

$$\Rightarrow P = i(\mathcal{E} - ir)$$

$$= \underbrace{i\mathcal{E}} - \underbrace{i^2 r}$$

power of
EMF

power dissipated
through internal
resistance.

Multiloop circuits

key thing to remember:

Kirchhoff current law -

the sum of currents entering


a junction is equal to the

sum of currents exiting it.



$$i_1 = i_2 + i_3$$

Consider the circuit

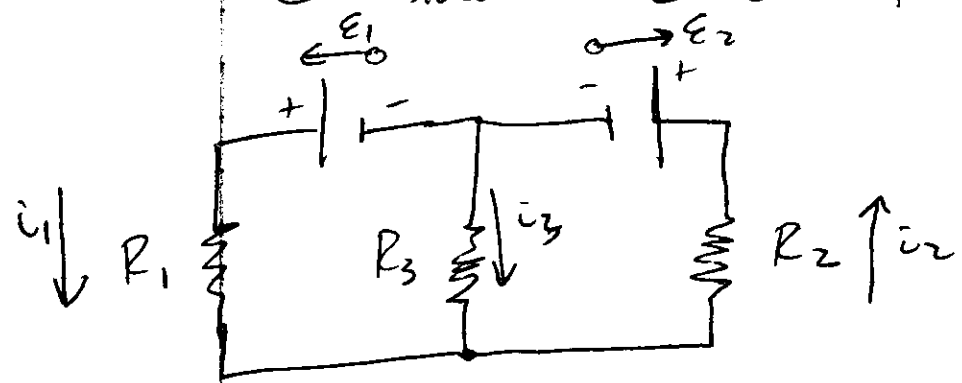

current law \Rightarrow $i_1 + i_3 = i_2$


going around loop 1 $E_1 - i_1 R_1 + i_3 R_3 = 0$

loop 2 $-i_3 R_3 - i_2 R_2 - E_2 = 0$


can solve for currents now...

10

Resistors in parallel

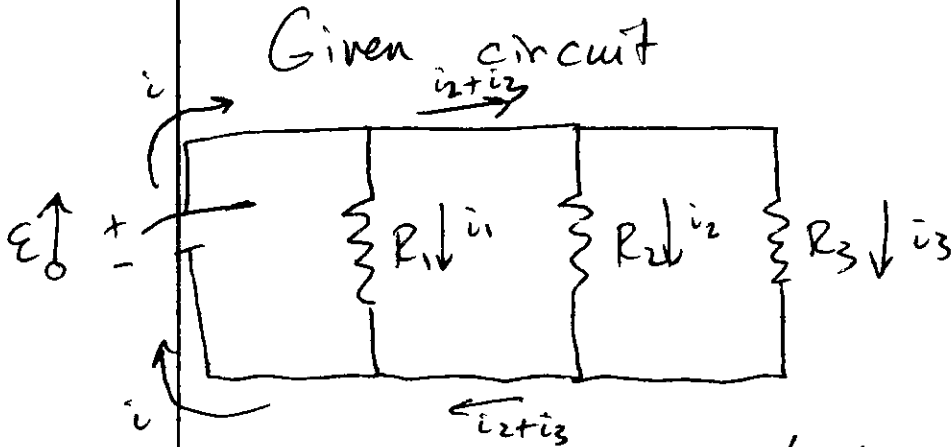

What is equivalent resistance?

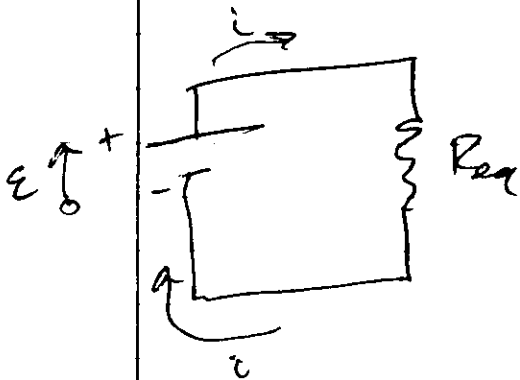

$$E - i_1 R_1 = 0$$

$$E - i_2 R_2 = 0$$

$$E - i_3 R_3 = 0$$

$$\Rightarrow i_1 = \frac{E}{R_1}$$

$$i_2 = \frac{E}{R_2}$$

$$i_3 = \frac{E}{R_3}$$

$$i = \frac{E}{R_{eq}}$$

But $i = i_1 + i_2 + i_3 \Rightarrow$

$$\frac{E}{R_{eq}} = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3} \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$