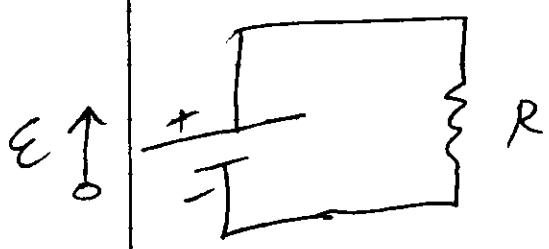


Lecture 21

①

15 OCT 2014


Review of last time:




EMF device w/ ~~EMF~~ \mathcal{E}
is like a battery.

$$V_a + \mathcal{E} - iR = V_a$$
$$\Rightarrow \mathcal{E} = iR$$

Resistors in Series:

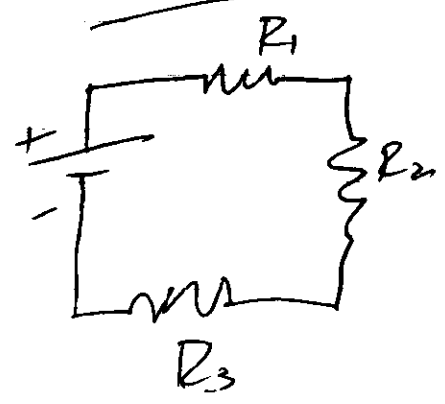


What is equivalent circuit?

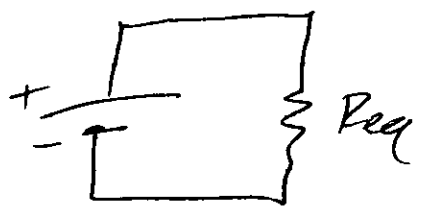


$$R_{eq} = R_1 + R_2 + R_3$$

Resistors in Parallel :

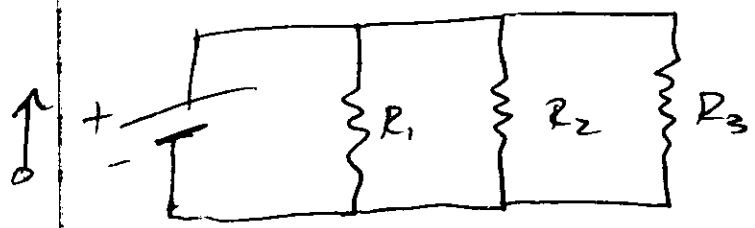


What is equivalent circuit ?

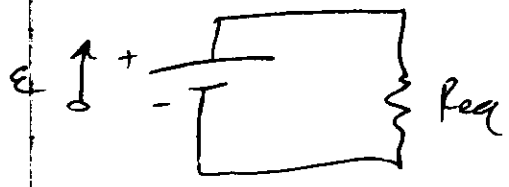

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

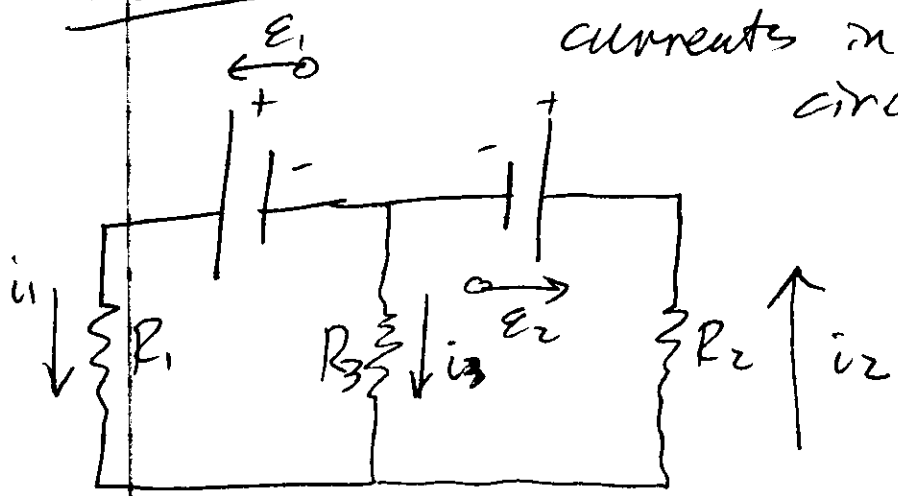QUESTION :

What are the three currents in the following circuit ?



$$i_1 + i_3 = i_2$$


$$E_2 + i_2 R_2 + i_3 R_3 = 0$$

$$E_1 - i_1 R_1 + i_3 R_3 = 0$$

3

QUESTION:


How to find equivalent circuit for

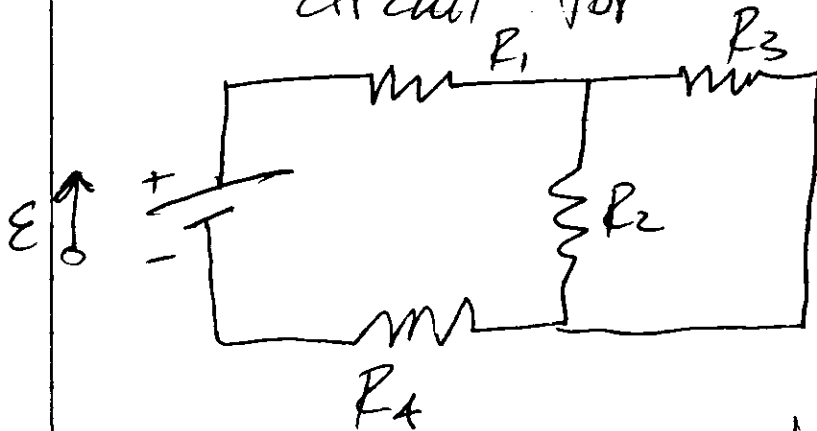

can then use this to figure out currents

1st step: R_2 + R_3 in parallel so
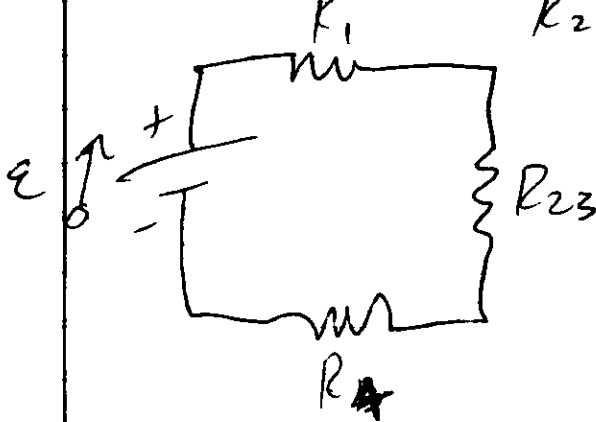
$$R_{23} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_2 R_3}{R_2 + R_3}$$



So current equals

$$\frac{\epsilon}{R_1 + R_{23} + R_4} = i$$

④

\Rightarrow potential drop across R_1

$$\text{is } i R_1$$

ϕ across R_{23} is $i R_{23}$

ϕ across R_4 is $i R_4$

but voltage across $R_2 + R_3$

is the same, so the

current through R_2

$$\text{is } \frac{i R_{23}}{R_2} \text{ of that}$$

$$\text{through } R_3 \text{ is } \frac{i R_{23}}{R_3}$$

5

Ammeter & Voltmeter


devices used to measure current & voltage, respectively

to measure current through a wire, "break it" & connect ammeter in -



important that resistance^{of ammeter} is very small so that it does not alter current.

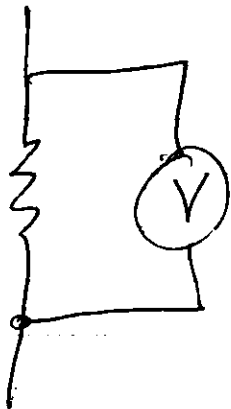
to measure voltage across a resistor use voltmeter as



important that resistance of voltmeter be much larger than that of resistor.

6

RC circuits

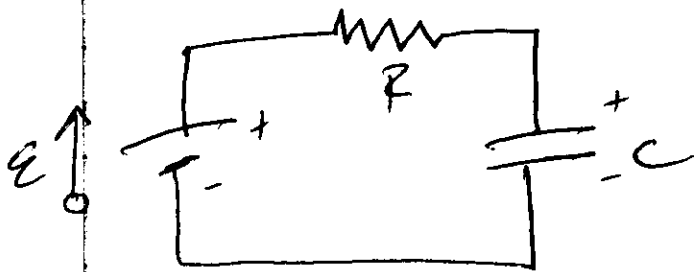

We know that when we connect the circuit, the capacitor charges up to a point where it is fully charged, & then current no longer flows.

QUESTION: How can we use the

loop rule to relate E , i , R ,
 q on capacitor
& C ?

$$E - iR - \frac{q}{C} = 0$$

\uparrow negative ^{b/c} of potential
difference across capacitor

7

cannot solve b/c two independent variables q & i , but

$$i = \frac{dq}{dt} \Rightarrow$$

$$E = R \frac{dq}{dt} + \frac{q}{C}$$

more explicitly, $E = R \frac{dq(t)}{dt} + \frac{q(t)}{C}$



This is a differential equation that we need to solve.

Initial condition is that $q=0$ @ $t=0$.

solution will be

$$q(t) = CE (1 - \exp\{-t/RC\})$$

so charge will look like

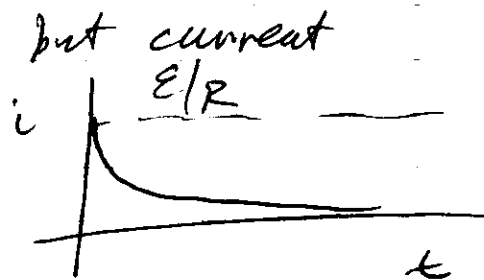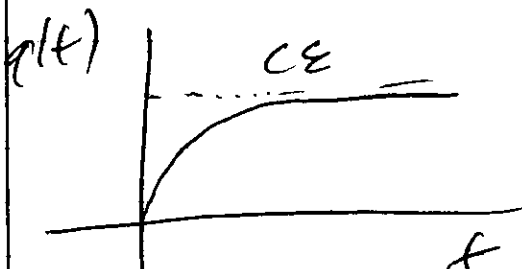

8

$$\begin{aligned}\frac{dq(t)}{dt} &= C \varepsilon \exp\left\{-t/RC\right\} \frac{1}{RC} \\ &= \frac{\varepsilon}{R} \exp\left\{-t/RC\right\}\end{aligned}$$

$\Rightarrow V(t)$ for capacitor is

$$V(t) = \frac{q(t)}{C} = \varepsilon (1 - \exp\{-t/RC\})$$

Why is $q(t)$ a solution?

$$\text{b/c } \varepsilon = R \frac{dq(t)}{dt} + \frac{q(t)}{C}$$

$$= R \cdot \frac{\varepsilon}{R} \exp\{-t/RC\} +$$

$$\varepsilon (1 - \exp\{-t/RC\})$$

$$= \varepsilon$$

so it satisfies.

Furthermore, initial condition $q(0) = 0$ is satisfied

9

RC is called the time constant

(it has dimensions of time
 $1 \Omega \times 1 F = 1 s$)

After ~~putting~~ a time $t = RC$,


charge is $C \mathcal{E} (1 - e^{-1})$

$$\approx (0.63) C \mathcal{E}$$

so after this time the ~~current~~
capacitor is 63% charged.

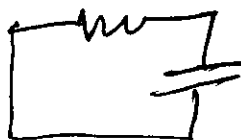D. is changing a capacitor

What if we change it +
then it's connect battery so
that



10

Then the same loop rule
gives

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$

∴ solution is

$$q = q_0 \exp\left\{-t/RC\right\}$$

where q_0 is initial charge
 $= CE$

∴ charge decreases exponentially
fast with time.

What about current?

$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right) \exp\left\{-t/RC\right\}$$

∴ current does as well. ...