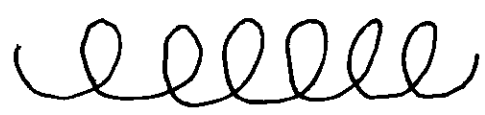


Lecture 30

7 NOV 2014

Consider a solenoid as the basic kind of inductor



establishing a current through the coils induces a magnetic flux Φ_B

the ~~flux~~ induced flux is proportional to the current (follows from discussion on solenoids)

$$i \propto \Phi_B$$

proportionality constant is called inductance L

if we also need # of turns & define L by

$$iL = N \Phi_B$$

where N is # of turns

(2)

$$\Rightarrow L = \frac{N\Phi_B}{i}$$

unit of inductance is the

$$\text{Henry} = \left[\frac{\text{T} \cdot \text{m}^2}{\text{A}} \right] \quad \text{b/c flux} \\ \text{current}$$

What is inductance for a solenoid?

Let n be # of turns per unit length & consider a length l

then for this length,

$$N\Phi_B = n l B A$$

where A is cross-sectional area

But before we found for a solenoid that $B = \mu_0 n i$

$$\Rightarrow L = \frac{N\Phi_B}{i} = \frac{n l B A}{\frac{B}{\mu_0 n}} = \mu_0 n^2 l A$$

$$\Rightarrow \frac{L}{l} = \mu_0 n^2 A$$

3

So inductance per unit length
only depends on geometry
(# of turns per unit length &
cross-sectional area)

Self-induction

a current in one coil produces
magnetic flux in another

- changing the current induces

an EMF according to

$$\text{Faraday's law } (\mathcal{E} = -\frac{d\Phi_B}{dt})$$

For a solenoid inductor, we have

$$N\Phi_B = Li$$

Faraday's law gives that

$$\mathcal{E}_L = -\frac{d(N\Phi_B)}{dt}$$

(induced EMF for inductor)

(4)



Combining these equations gives

$$\mathcal{E}_L = -L \frac{di}{dt}$$

direction of induced EMF


opposes direction of increasing current

For a picture, we have

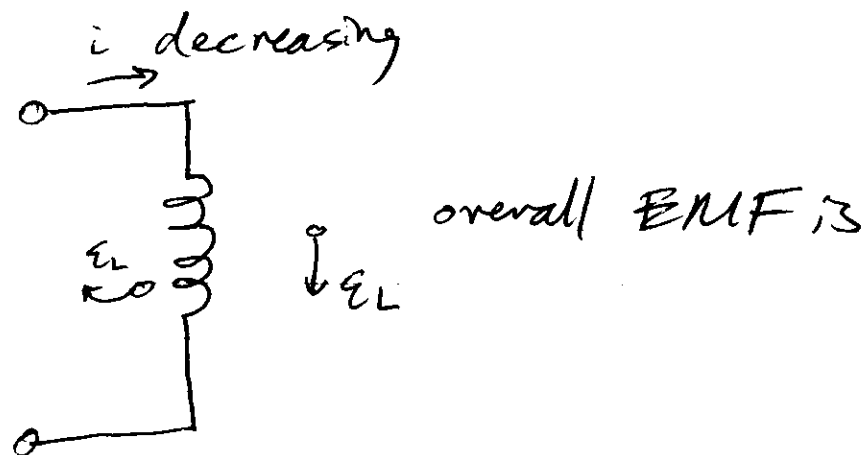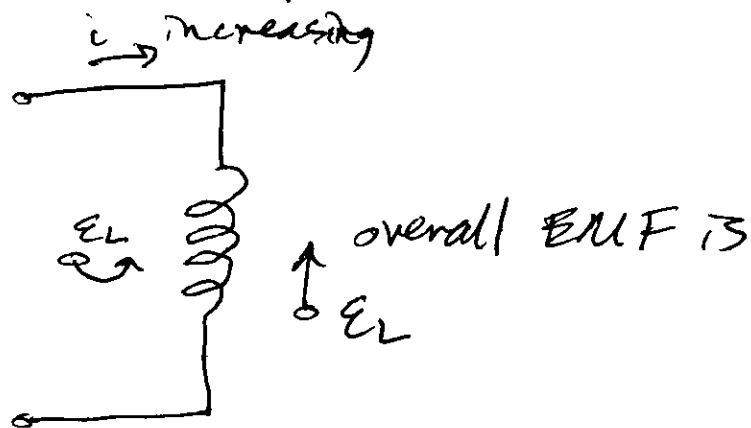

5

RL circuits

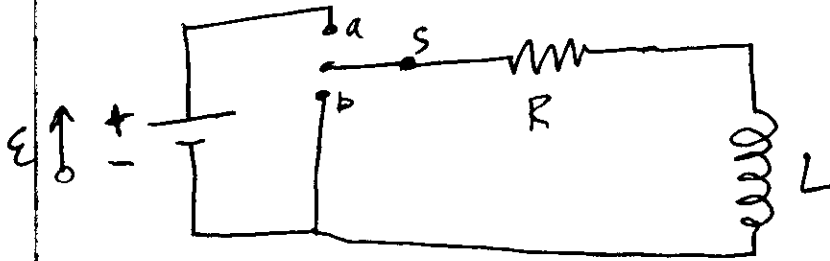

When the switch is flipped to a,
there is a rapid increase in current
→ through resistor.

Since the inductor is present, it ^{↑ current} ~~acts as~~ has an induced EMF
that opposes direction of current.

So the current through the resistor
is initially less than \mathcal{E}/R

(which is what it would be if
the inductor were not there)

(6)

After some time, the ~~current~~ change in current gets smaller & so the induced EMF of inductor gets smaller as well

$$\left(\mathcal{E}_L = -L \frac{di}{dt} \right)$$


Rule of thumb: After switch is closed,

At $t=0$ inductor acts like a broken wire

At $t=\infty$ inductor acts like an ordinary wire

Simple example to apply this ~~rule~~ rule of thumb


QUESTION:

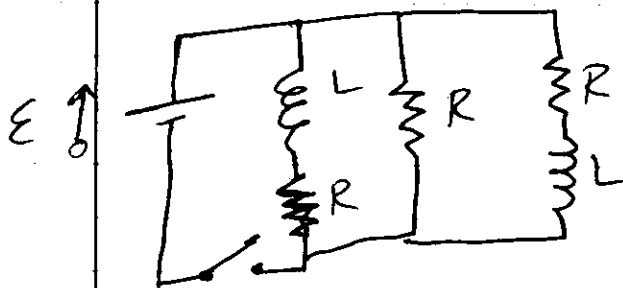

What is current through battery just after switch is closed?

7

can picture as

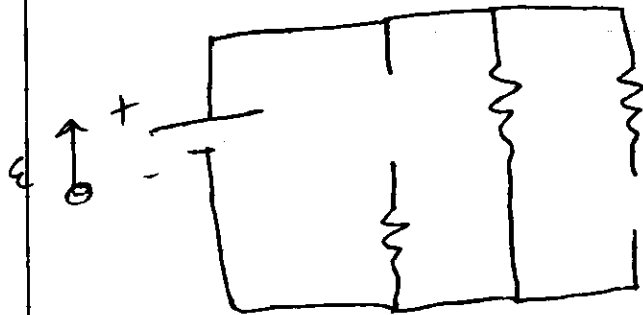


so circuit is just



$$I = \frac{\mathcal{E}}{R}$$

After a long time

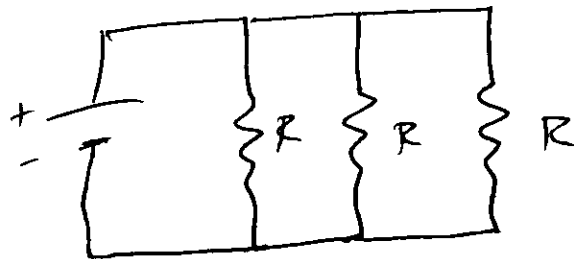


these are in parallel, so



$$I = \frac{\mathcal{E}}{R/3}$$

8

Solve the RL circuit equation

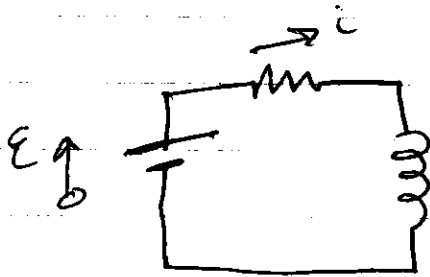

loop rule

$$\mathcal{E} - iR - L \frac{di}{dt} = 0$$

↑ minus sign because direction of EMF opposes direction of increasing current

$$\mathcal{E} = iR + L \frac{di}{dt}$$

differential equation w/ initial condition $i(0) = 0$

9

Solution is

$$i(t) = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$

Why solution? $i(0) = 0$

$$\& \quad \frac{di(t)}{dt} = \frac{\mathcal{E}}{L} e^{-Rt/L}$$

$$iR = \mathcal{E} (1 - e^{-Rt/L})$$

$$L \frac{di(t)}{dt} = \mathcal{E} e^{-Rt/L}$$

summing them gives \mathcal{E}

Substitute in to match w/ qualitative behavior:

$$i(0) = 0 \quad \text{so}$$

no current going through resistor initially &

$i(s)$ is small b/c of induced opposing EMF

(10)

time constant for
circuit is L/R

this indicates how long it takes

for current to reach certain ~~value~~
fractions of its final value.

If switch is thrown to (b)
(disconnecting battery) then the
circuit equation becomes

$$L \frac{di}{dt} + iR = 0$$

↳ solution is

$$i(t) = \frac{E}{R} e^{-tR/L}$$

so current doesn't immediately drop
off but decays exponentially
to zero.