


Lecture 31

10 Nov 2014


we've seen RC circuits & RL circuits.

What about LC circuits?

Consider the following

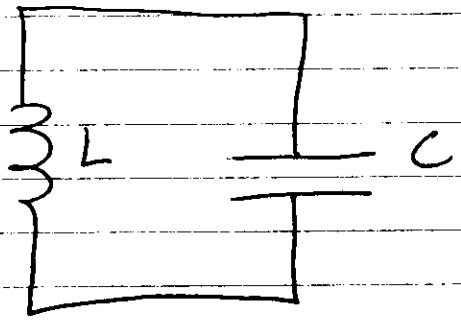

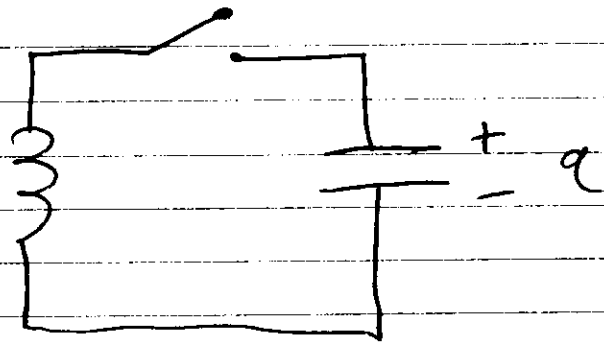
Suppose capacitor is initially charged before closing a switch:




energy stored in electric field of capacitor is $\frac{q^2}{2C}$

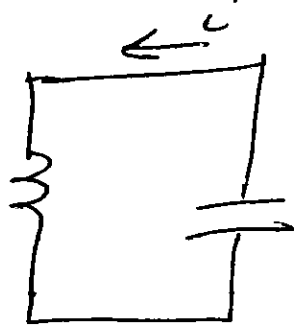(2)

After closing switch,
increasing current goes from positive
to negative



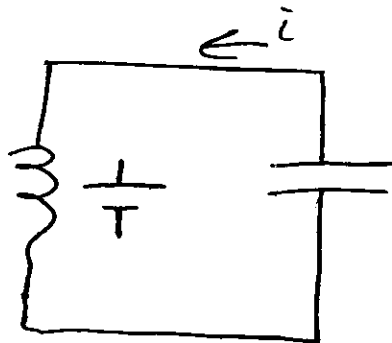But the inductor sets up
an EMF to oppose the
direction of increasing current




(it resists a changing
current)

electrical energy
stored in capacitor
is being converted
to magnetic energy
stored in magnetic
field of the inductor

3

Eventually the capacitor loses all of its charge & current through the inductor is at its maximum. (All electrical energy has been converted to magnetic energy)

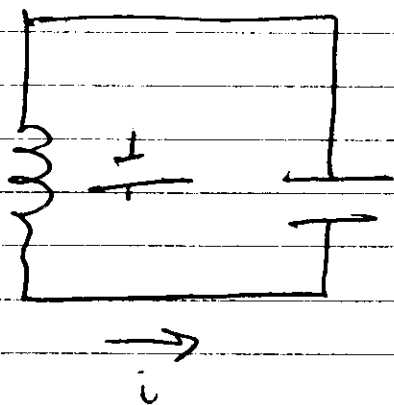
The current through the inductor starts decreasing, but then ~~the~~ the inductor sets up an EMF in the direction of decreasing current, so picture looks like



The energy needed to do this is coming from stored magnetic energy

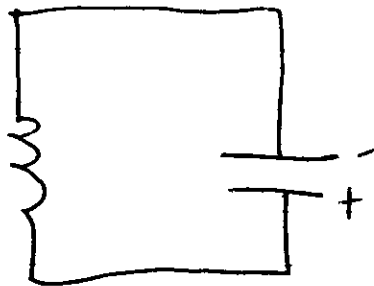(4)

So this current transfers positive charge to the bottom plate of capacitor and eventually the picture becomes



so that all magnetic energy goes to electrical energy stored in capacitor.

Things continue as in beginning but in opposite way


behavior is like that of a harmonic oscillator.

(5)

How to describe this mathematically?

use the loop rule for
beginning scenario
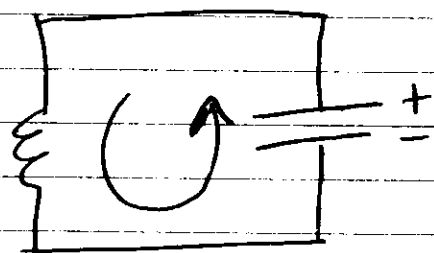
$$q = VC + \mathcal{E}_L = -L \frac{di}{dt}$$



Question: What is loop rule?

$$-\frac{q}{C} - L \frac{di}{dt} = 0$$

$$\text{but } i = \frac{dq}{dt} \Rightarrow \frac{di}{dt} = \frac{d^2q}{dt^2}$$

$$\Rightarrow \frac{q(t)}{C} + L \frac{d^2q(t)}{dt^2} = 0$$

(6)

This is a differential equation describing dynamics of current & charge in circuit.

This is exactly analogous to a mass on a frictionless spring.

guess a solution of the form

$$q(t) = Q \cos(\omega t + \phi)$$

where Q is amplitude,

ω is angular frequency, &

ϕ is phase.

then
$$i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$

~~so~~ so amplitude for current is

$$I = \omega Q \text{ so}$$

$$i = -I \sin(\omega t + \phi)$$

7

$$\frac{d^2 q}{dt^2} = -\omega^2 Q \cos(\omega t + \phi)$$

\Rightarrow substituting back in gives

$$\frac{Q}{C} \cos(\omega t + \phi)$$

$$-L\omega^2 Q \cos(\omega t + \phi) = 0$$

solution occurs when

$$\omega = \frac{1}{\sqrt{LC}}$$

initial conditions give the phase ϕ .

Question:

What is electrical energy stored in capacitor at any given time?

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$

8

magnetic energy in inductor \mathcal{E}

$$U_B = \frac{1}{2} Li^2 = \frac{1}{2} L\omega^2 Q^2 \sin^2(\omega t + \phi)$$

energy oscillates back & forth

b/c \sin & \cos are out of phase by 90° .

this is all analogous to a mass moving on a spring

~~the~~