

Lecture 10


①

- circuit model of computation
- a circuit is a directed, acyclic graph

Examples of basic logic gates

AND

truth table

 

x	y	$x \wedge y$
0	0	0
0	1	0
1	0	0
1	1	1

Notice that the gate is irreversible

i.e., from outputs we cannot figure out inputs (0 @ output has 00, 01, & 10 as input)

Thus information is erased
when applying this logic gate


Aside: Landauer established a
fundamental connection between
physics & information w/
his erasure principle:

erasing 1 bit of information
leads to ^{at least} $kT \ln 2$ units of
heat to be dissipated to
the environment

in q. computing, we are interested
in reversible gates in order to
correspond w/ unitary evolution
& to maintain superpositions

other basic gates


OR

 

x	y	$x \vee y$
0	0	0
0	1	1
1	0	1
1	1	1

irreversible

XOR

 

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

irreversible

binary addition

can be made reversible by
 copying input x to output
 & then we get CNOT gate.

NOT



x	\bar{x}
0	1
1	0

reversible

(4)

Fundamental Universality Theorem
for computation w/ circuits:

can compute any Boolean

function $f: \{0,1\}^n \rightarrow \{0,1\}^m$


using a circuit composed
of the aforementioned gates,
in addition to copy & swap.

Important caveat: this theorem
does not imply that every
function is efficiently computable.

So we need to separate those
functions that are efficiently
computable from those that are not.

5

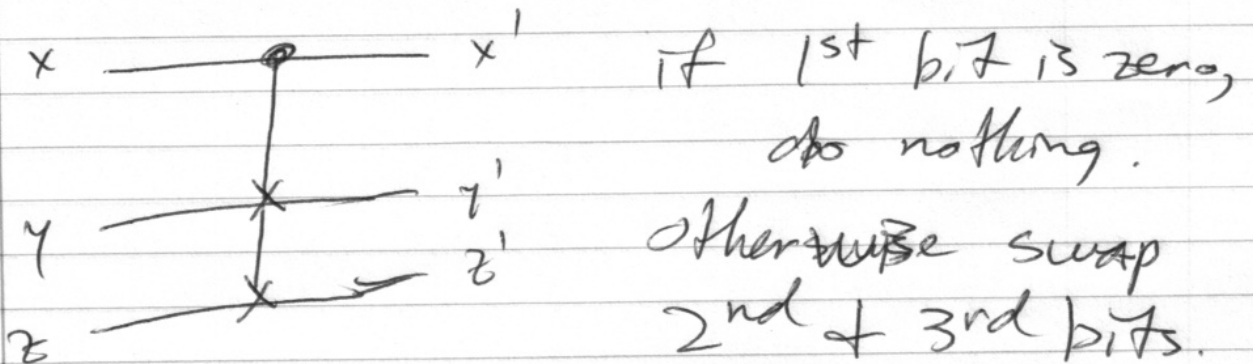let us now discuss reversible
computation. Basic logic gate
here is the controlled SWAP
(c-SWAP)



truth table


x	y	z	x'	y'	z'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	1	1	1

reversible gate & in fact we already
used the quantum version


(6)

This c-SWAP gate is self-inverse


It can simulate AND as follows:

 

can simulate NOT

 

simulate OR

 

So AND & NOT can be simulated

w/ c-SWAP & vice versa

we can always thus promote a general circuit to a reversible one, by replacing every gate w/ c-SWAP

7


- This is a general principle that we can also use when promoting classical Boolean circuits to quantum circuits, which can be used in basic q. algorithms like Deutsch - Jozsa & Grover
- idea is to 1st make circuit reversible by replacing w/ c-SWAPs & then by understanding c-SWAPs as q. c-SWAPs, we have a q. circuit.
- However, when doing so, we end up w/ unwanted "garbage" bits.
- In the q. case, we have to clean them up & the way to do so is called uncomputation

8


Observe in the examples above that we end up w/ extra bits besides inputs & results of computation. These are called garbage bits.

How to do this?

Model original circuit as

 

 After being promoted to reversible circuit, it has the form




↑
auxiliary bits

↑
garbage bits


(required to be initialized to certain values in the simulation's presented)

9

 can realize values of a
via NOT gates acting on 0




to clean up consider the following

 

↑ reverse of R_f

then full circuit is

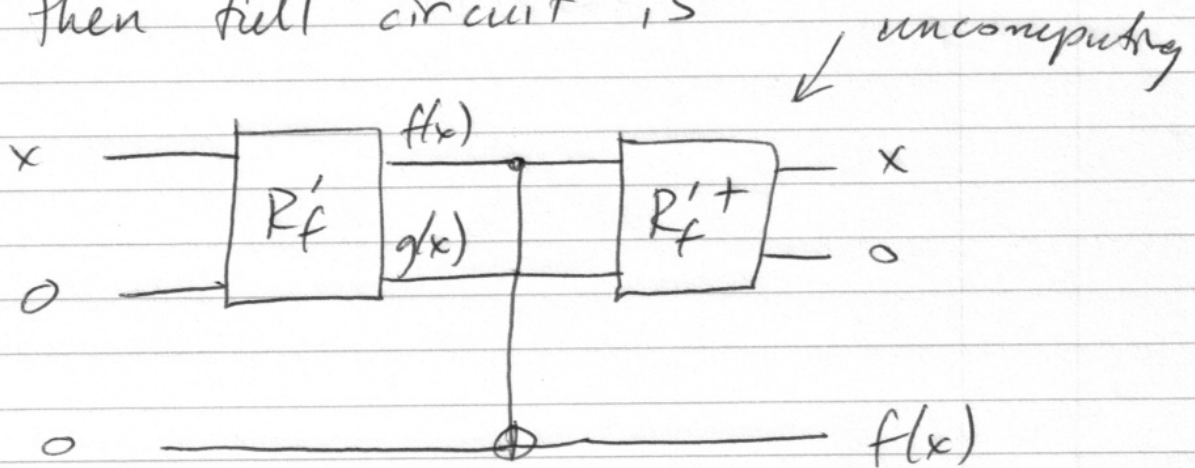

↑ sequence of CNOT gates
to copy the answer

We can then consider this to be a q . circuit, call it U_f , w/ the following action on standard basis states

$$U_f |x\rangle |0\rangle |0\rangle = |x\rangle |0\rangle |f(x)\rangle$$

It acts on superpositions as follows

$$\begin{aligned}
U_f |+\rangle^{\otimes n} |0\rangle |0\rangle &= \frac{1}{\sqrt{2^n}} \sum_{x \in \{0,1\}^n} U_f |x\rangle |0\rangle |0\rangle \\
&= \frac{1}{\sqrt{2^n}} \sum_x |x\rangle |0\rangle |f(x)\rangle
\end{aligned}$$

the entanglement between 1st & 3rd registers is the right kind of entanglement for q . algorithms

(11)

If we had not done the cleanup, the resulting state from 1st R_f' & cvars would be

$$|+\rangle^{\otimes n} |0\rangle |0\rangle \rightarrow$$

$$\frac{1}{\sqrt{2^n}} \sum_x |x\rangle |g(x)\rangle |f(x)\rangle$$

leaving undesired entanglement w/ 2nd register of garbage bits & would mess up q. algorithms that call functions like this.